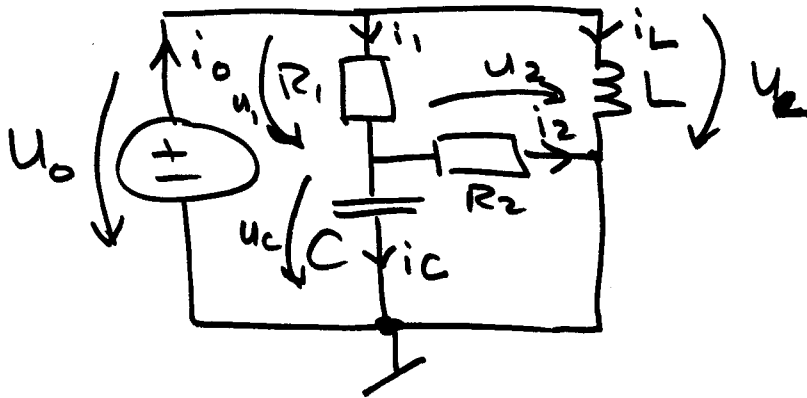


Modeling circuits in the time domain

Given a circuit:



We name all voltages and currents. Since we have n -branches in the circuit, there are now $2n$ variables.

\Rightarrow We need $2n$ equations to compute them.

We start with the elemental laws of each branch:

$$U_0 = f(t)$$

$$U_1 = R_1 \cdot i_1$$

$$U_2 = R_2 \cdot i_2$$

$$i_C = C \cdot \frac{dU_C}{dt}$$

$$U_L = L \cdot \frac{di_L}{dt}$$

} n equations
(one per branch)

We then formulate Kirchhoff's Voltage law for each mesh:

$$U_0 = U_1 + U_C$$

$$U_L = U_1 + U_2$$

$$U_C = U_2$$

and Kirchhoff's current law for each node except the ground node:

$$i_0 = i_1 + i_L$$

$$i_1 = i_2 + i_C$$

Since in every circuit:

$$\#_{\text{meshes}} + \#_{\text{nodes}} \equiv \#_{\text{branches}} + 1$$

we now got $2n$ equations.

We assume the state variables (outputs of integrators) to be known. We underline all known variables.

We now visit each equation. If an equation only contains one unknown, we solve for that unknown. If an unknown shows up in only one unused equation, we need to solve for it from that equation. We place the variables we solve for in square brackets.

- 53 -

$$[U_0] = f(t)$$

$$u_1 = R_1 \cdot [i_1]$$

$$u_2 = R_2 \cdot [i_2]$$

$$i_c = C \cdot \left[\frac{du_c}{dt} \right]$$

$$u_L = L \cdot \left[\frac{di_L}{dt} \right]$$

$$u_0 = [u_1] + u_c$$

$$[u_L] = u_1 + u_2$$

$$u_c = [u_2]$$

$$[i_0] = i_1 + i_L$$

$$i_1 = i_2 + [i_c]$$

$$\Rightarrow U_0 = f(t)$$

$$i_1 = u_1 / R_1$$

$$i_2 = u_2 / R_2$$

$$\frac{du_c}{dt} = i_c / C$$

$$\frac{di_L}{dt} = u_L / L$$

$$u_1 = u_0 - u_c$$

$$u_L = u_1 + u_2$$

$$u_2 = u_c$$

$$i_0 = i_1 + i_L$$

$$i_c = i_1 - i_2$$

are the solved equations.

We can now construct a state-space model:

$$u = u_0$$

$$x_1 = u_c$$

$$x_2 = i_L$$

$$y = u_2 \quad (\text{why not!})$$

$$\dot{x}_1 = \frac{dx_1}{dt} = \frac{du_c}{dt} = \frac{1}{C} \cdot i_c = \frac{1}{C} \cdot i_1 - \frac{1}{C} \cdot i_2$$

$$= \frac{1}{R_1 C} \cdot u_1 - \frac{1}{R_2 C} \cdot u_2$$

$$= \frac{1}{R_1 C} \cdot u_0 - \frac{1}{R_1 C} \cdot u_c - \frac{1}{R_2 C} \cdot u_c$$

$$= \frac{1}{R_1 C} \cdot u - \frac{1}{C} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) x_1$$

$$\dot{x}_2 = \frac{dx_2}{dt} = \frac{di_L}{dt} = \frac{1}{L} \cdot u_L = \frac{1}{L} \cdot u_1 + \frac{1}{L} \cdot u_2$$

$$= \frac{1}{L} \cdot u_0 - \cancel{\frac{1}{L} \cdot u_c} + \cancel{\frac{1}{L} \cdot u_c} = \frac{1}{L} \cdot u$$

$$y = u_2 = u_c = x_1$$

- 55 -

$$\left| \begin{array}{l} \dot{x}_1 = -\frac{R_1 + R_2}{C(R_1 R_2)} x_1 + \frac{1}{R_1 C} u \\ \dot{x}_2 = \frac{1}{L} u \\ y = x_1 \end{array} \right|$$

In matrix form:

$$\left| \begin{array}{l} \dot{\underline{x}} = \begin{bmatrix} -\frac{R_1 + R_2}{R_1 R_2 C} & \emptyset \\ \emptyset & \emptyset \end{bmatrix} \underline{x} + \begin{bmatrix} \frac{1}{R_1 C} \\ \frac{1}{L} \end{bmatrix} u \\ y = \begin{bmatrix} 1 & \emptyset \end{bmatrix} \underline{x} + \begin{bmatrix} \emptyset \end{bmatrix} u \end{array} \right|$$

Of course, if we are only interested in u_2 , we wouldn't need to compute i_L at all.

-56-

$$\left| \begin{array}{l} x_1^o = -\frac{R_1 + R_2}{R_1 R_2 C} x_1 + \frac{1}{R_1 C} u \\ y = x_1 \end{array} \right|$$

$$\Rightarrow \left| \begin{array}{l} x_1^o = \left[-\frac{R_1 + R_2}{R_1 R_2 C} \right] x_1 + \left[\frac{1}{R_1 C} \right] u \\ y = \left[\quad 1 \quad \right] x_1 + \left[\emptyset \right] u \end{array} \right|$$
